

# IMPLEMENTATION OF BOOLEAN LOGIC USING ARDUINO

K. Azmathulla


iamazmath771@gmail.com

COMET.FWC017

## Future Wireless Communication (FWC) ASSIGNMENT

July 07, 2025

### Abstract

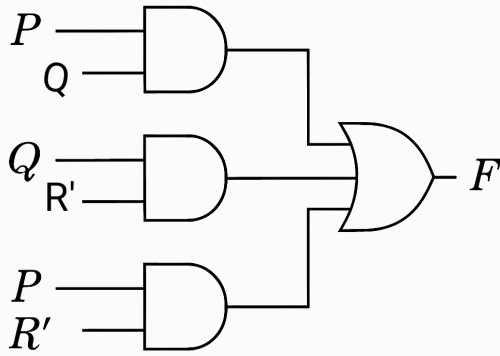

(GATE 2010, Question No.6: The minterm expression of  $f(P, Q, R) = PQ + QR' + PR'$  is ? By using Arduino)

### 1. Components

Component	Qty
Arduino UNO Board	1
USB Cable (Type B)	1
Push Buttons	3
LEDs	1
220 $\Omega$ Resistors	3
Jumper Wires (M-M)	10
Breadboard	1
Android Mobile with Arduinodroid App	1

Table 1: List of components used

### 2. Setup and Connections

1. Connect push buttons to D2, D3, D4 for P, Q, R.
2. Add pull-down resistors to each input.
3. Connect an LED to pin D13 via a 220 $\Omega$  resistor.
4. Common ground for buttons and LED.
5. Power Arduino via USB and Arduinodroid app.

### 3. Steps for Implementation

1. Complete the circuit connections.
2. Connect Arduino to mobile via USB.
3. Open Arduinodroid, select board and port.
4. Open, save, compile and upload code.

### 4. Truth Table

P	Q	R	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

## 5. Boolean Expression Simplification

$$F = PQ + PR' + Q R'$$

## 6. Input and Output Pins

- P (Input) – D2
- Q (Input) – D3
- R (Input) – D4
- F (Output LED) – D13

